

- 1) A power plant is built to provide a 40MW electric power for the city. To do so it provides a potential difference of 25kV AC and is connected to the city via  $10\ \Omega$  wires. Calculate how much of the electric power is dissipated in the wires providing the required current. (you may neglect potential drop on the wires)